



BY WILLIAM I. ORR, W6SAI

The Doerle Shortwave Receiver

It's December, 1931. New York City is snowbound after weeks of bad weather and is in the midst of a paralyzing financial depression. Over 30 per cent of the work force is unemployed. The stock market has plunged to new depths of gloom. The radio industry is at a standstill. The broadcast-set construction boom had collapsed, and the ac-operated receiver had not yet reached the market in quantity.

In the lower New York City area, the many small radio distributors were in trouble. Some of them closed their doors forever, and the ones that had managed to stay open had few customers. Something was needed to break out of the dismal cycle of bad weather, unemployment, and economic stagnation. For the nation as a whole the bad weather would soon dissipate, but the economic picture looked black — all except for a handful of small, grimy, radio stores in the Vessey-Cortland-Dey-street area that had unexpectedly stumbled onto a gold mine that proved to be their salvation for a few years.

Shortwave radio! It caught the public's fancy some time in 1931. Young men, unemployed,

with plenty of time on their hands, started the craze. For only a few dollars you could buy a small shortwave receiver that would literally "pull in the world." And the interest was aroused by an obscure radio fan in Oakland, California, who popularized a two-tube regenerative receiver.

Little is known today about Walter C. Doerle of Oakland. He's not listed in the telephone book, and he faded from fame about 1934. In any event, he designed and built a simple two-tube shortwave receiver and wrote about it for publication in the December, 1931, issue of *Short Wave Craft* magazine. The little set was inexpensive to build and sure-

fire in operation. This was the right radio at the right time!

No doubt Doerle was surprised at the explosive interest in his little radio! Requests for more information poured into the magazine, along with glowing reports of how the inexpensive, easy-to-build radio pulled in stations all over the globe. The Doerle receiver became famous overnight.

The Doerle receiver

After the original article on the receiver, Walter Doerle gradually faded from the scene. He wrote one or two other radio articles, but his fame was quickly taken over by a group of small radio stores on New York City's "radio row," who knew a good thing when they saw it. It's not known if Doerle made any financial profit from his radio, but his name became a household word for any simple shortwave set. "Doerle clubs" sprang up around the country and "Doerle circuits" were sold as kits and as complete radios.

Amazingly, most radio hams had never heard of the Doerle receiver. It seemed to be advertised only in radio magazines catering to the

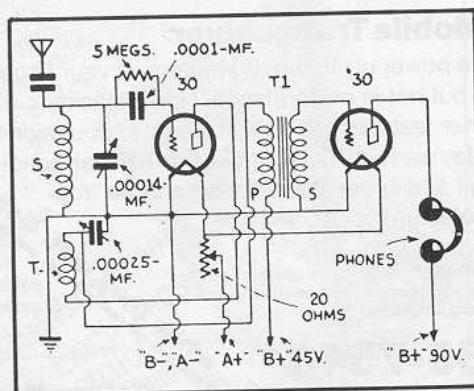


Fig. 1. Circuit used by Mr. Doerle for the 2-tube "globe circler."

shortwave listener (SWL) and the home constructor. But as shortwave listening became a popular pastime (much as CB radio is today), the Doerle designs were duplicated by the uncounted thousands.

The Doerle receiver was simplicity in itself (Fig. 1). It was a simple, two-tube regenerative receiver. One tube served as a regenerative detector and one tube as an audio amplifier. An "A" battery for the filament supply, and 90 volts of "B" battery, were required to run the receiver. Figs. 2 and 3 show modified versions of the receiver.

Originally designed for the low-drain type 30 tubes, the receiver worked equally well with the cheap, plentiful type 201A tubes and a second-hand 6-Volt automobile battery for the filament supply. And later, the Doerle circuit would be redesigned for the new type 227 ac-operated triode tubes.

Building the Doerle receiver

Most builders ignored the Doerle kits, even though they sold for less than five dollars for the economy-model receiver. Two tubes could be obtained for less than 25 cents at a rummage sale or radio junk shop. The audio transformer? Free, or perhaps 15 cents from the same source. Tube sockets were easy to obtain and cheap, even if bought new. Coils?



Doerle type regenerative receiver built from a 1938 kit. This battery-operated receiver uses a 1F4G as a detector, a 1H5G audio amplifier, and a 1C5G second audio stage. The 1F4G detector is in the center with a metal shield over the tube. Shortwave spectrum from 10 to 200 meters is covered with four plug-in coils. When wired up, the receiver worked right off the bat!

Wind them on bases from burned-out tubes. And the tuning condensers* could be bought new for less than a dollar, or could be cut down from larger condensers

*Yep, they were known as condensers in those days. Today we call 'em capacitors. **Editor.**

salvaged from an old battery receiver.

According to the pictorial drawing, the Doerle was built on a wooden base: plywood or "breadboard," measuring about 203 by 305 mm (8 by 12 inches). That gave plenty of room for parts. The parts were arranged so that the panel was reason-

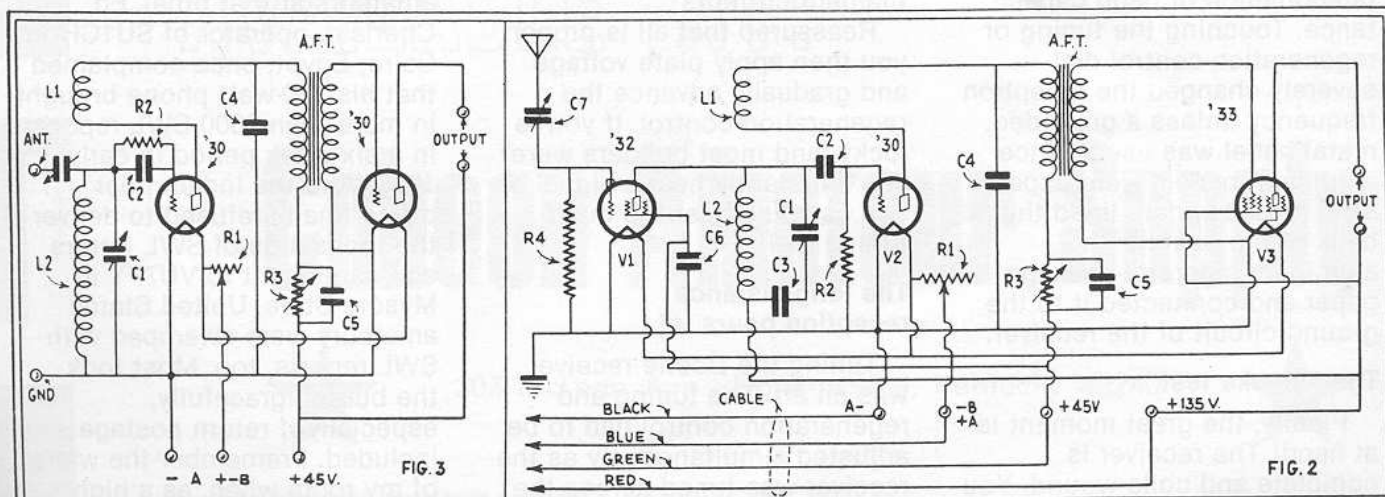


Fig. 2. The same two-tube receiver shows up in the schematic diagram at left, but with a few parts changes — note the variable coupling capacitor from the antenna terminal. Inevitably, the circuit was adapted for mobile use, shown at right with an rf amplifier ahead of the detector.

HARRISON RADIO CO.

★ QUALITY
★ MERCHANDISE

★ LOWEST
★ PRICES


★ REAL
★ SERVICE

★ EVERYTHING
★ GUARANTEED

Now!

The Improved Doerle 12,500 Mile Two Tube Short Wave Receiver

\$4.75

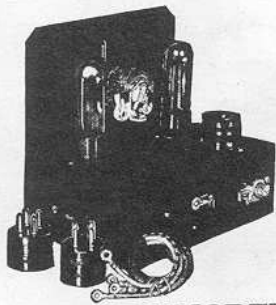

DC MODEL

Uses two 230 tubes. Batteries required are two dry cells (for a 2-volt storage cell) and two 45 volt B Batteries. If you have a 6-volt storage battery you may use 201-A's.

COMPLETE KIT \$4.75
Coils Wound 50c extra

ACCESSORIES

234 volt Filament Transformers, 95c. Heavy Duty, \$1.25. RCA Licensed TUBES. Fully guaranteed for three months. 230-75c. 201-A-39c. 227-46c. 50-60c. 280-45c. Other types at lowest prices. Large Dry Cells-29c. Large 45 volt B Batteries-50c. Imported light weight phones-\$1.35. Better grade, very sensitive, \$1.75.

AC MODEL

Uses two of the new type 56 tubes or two 27's. Power is obtained from the Model ED pack listed below or from any good eliminator delivering 90-200 volts and 234 volts. Or it may be run on a 234 volt filament transformer and two 45 volt Batteries.

COMPLETE KIT \$4.95
Coils Wound 50c extra

Either set or power pack completely wired and tested—\$2.25.

MODEL ED Power Pack—Delivers all power for AC Receiver. Heavy transformer and extra filtering insures quiet reception on short waves. Plugs into 110 volt, 60 cycle house line. Stamped metal chassis. Uses a 280 tube.

COMPLETE KIT \$4.85
For 110 volt, 25 cycle—\$5.85

Harrison Radio Company sold a Doerle receiver kit for less than five dollars. To save cost, regeneration was controlled by varying the detector plate voltage by potentiometer R3. The feedback capacitor, C4, was fixed.

ably symmetrical. The antenna coupling capacitor (oops! condenser) was cut from two small sheets of brass, or from a tin can if brass wasn't available.

Rarely mentioned was the phenomenon of hand capacitance. Touching the tuning or regeneration-control dial severely changed the reception frequency unless a grounded, metal panel was used. Since aluminum panels were expensive, most builders lined the back of the panel with aluminum cigarette-package paper and connected it to the ground circuit of the receiver.

The "smoke test"

Finally, the great moment is at hand! The receiver is complete and coils wound. You apply filament voltage carefully and examine the type 30 tubes in a darkened room to make sure the filaments are lighted.

A recheck of the wiring is usually necessary at this point, as inadvertent application of the B voltage to the filament circuit guarantees instant burnout of the two tubes, each of which draws only 60 mA of filament current.

Reassured that all is proper, you then apply plate voltage and gradually advance the regeneration control. If you're lucky (and most builders were) you'll instantly hear a signal or two as you adjust the main tuning dial.

The long-distance reception pours in!


Tuning the Doerle receiver was an art. The tuning and regeneration control had to be adjusted simultaneously as the receiver was tuned across the band. Too little regeneration meant no signal; too much meant a howl in the headphones. The adjustment of the

antenna capacitor was attempted, too — the plates being bent back and forth in relation to each other. More daring experimenters tried various values of "grid leak" (grid resistor). From 2 to 5 megohms seemed about right.

Once the tuning technique was established, the world was at the fingertips of the listener. Old standbys such as Rugby, England; VK2ME and VK3ME in Australia; and HVJ in the Vatican poured in along with lesser lights such as PCJ in Holland and VE9GW in Canada. The most sought-after station was a home-built 7-1/2 watt broadcaster in Costa Rica, on the air with a call "borrowed" from the U.S. Navy. The listener who heard NRH in Heredia, Costa Rica, was lucky indeed.

When SWling was a fine art

Unlike today, radio amateurs in the prewar era received SWL cards from all over the world. Since ssb was unknown in those dear dead days, amateurs used simple amplitude modulation (a-m) which could be easily received on a simple Doerle receiver (just reduce the regeneration control). Collecting SWL reports was a hobby that was probably greater than amateur radio (there were about 30000 amateurs at that time). Ed Chorlain, operator of SU1CH in Cairo, Egypt, once complained that his 150-watt phone brought in more than 3000 SWL reports in a six-week period in early 1935! And the Indian post office finally refused to deliver the thousands of SWL letters and cards sent to VU7FY in Mysore State. United States amateurs were swamped with SWL reports, too. Most took the burden gracefully, especially if return postage was included. I remember the walls of my room when, as a high-school student, I roamed the shortwave bands as an eager SWL. When I got my ham ticket, I stripped the walls of

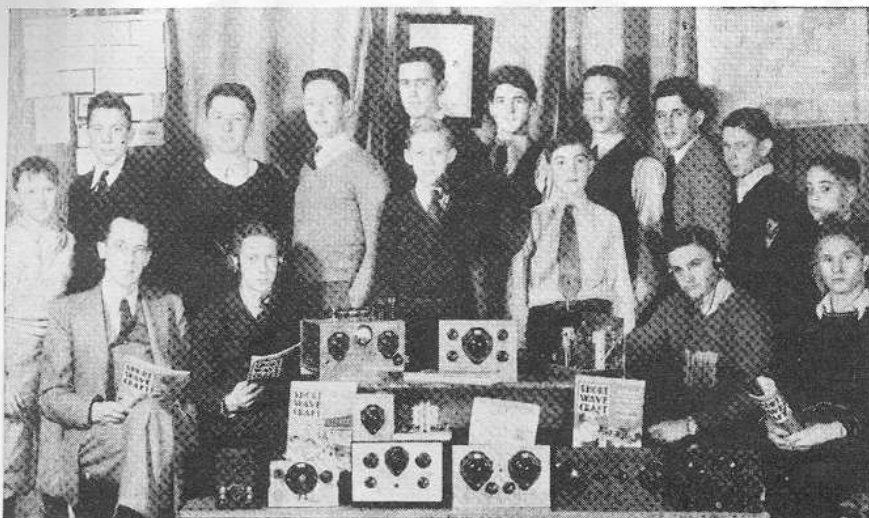

Doerle Radio Clubs sprang up all over the country in the 1930s. Homebuilt shortwave radio receivers were the rage, especially among the high-school set. This 1935 photograph shows the radio club of the Waupun High School of Wapun, Wisconsin. (Photo reproduced from *Short Wave Craft* magazine).

SWL cards, hoping to fill them with *real* QSLs from the contacts I hoped to make.

The Doerle becomes an industry

After the original excitement,

the Doerle circuit gave way to more exotic receivers. Three-, four-, five- and six-tube Doerle receivers appeared on the market, some rigged up in good-looking, crackle-finished metal cabinets. Most, however,

were merely the original circuit adapted to ac, with audio stages added to work a loud speaker. But they remained the first receiver of thousands of shortwave enthusiasts, many of whom became radio amateurs after their initial, thrilling exposure to shortwave radio through the sure-fire Doerle circuit.

By 1938 the Doerle fad had expired. The two-tube regenerative receiver, while still built by some beginners, was eclipsed by low-cost shortwave superheterodyne receivers. Modeled after the inexpensive broadcast receivers, the little superhets quickly took over the shortwave beginner's market. The depression was fading, more money was changing hands, and the radio enthusiast could afford a more expensive receiver. Soon the Doerle circuit was forgotten. But it had done its part to sustain the New York radio industry when the days were black and the future insecure.

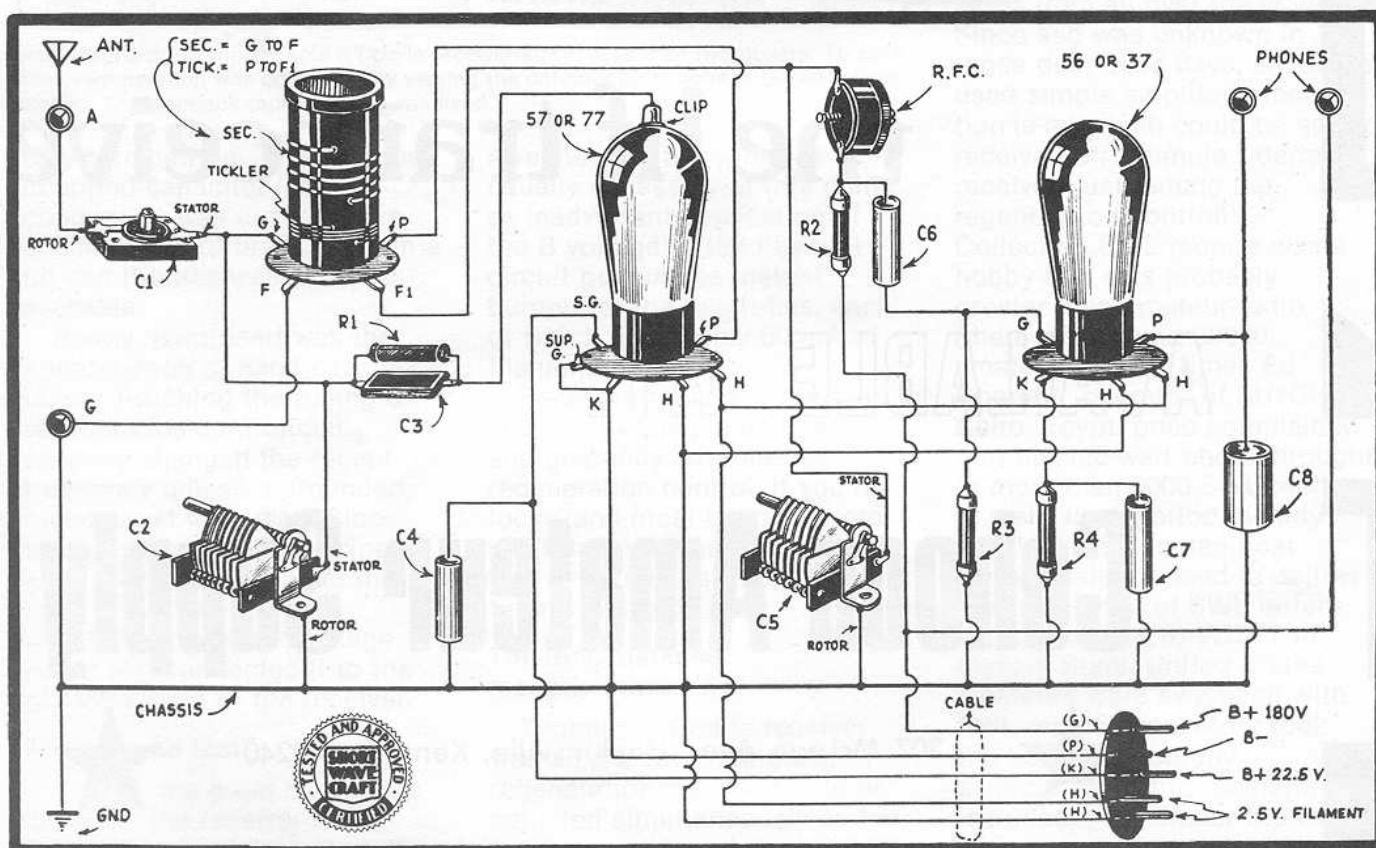


Fig. 3. The schematic diagram is typical of those seen in the early 1930s, and experimenters were helped by the clear picturized diagram" like the one above. Tube sockets were used for the plug-in coil forms, and carried their original filament, grid, and plate designations as a means of identifying where the wires were to be connected. Note the seal of approval of *Short Wave Craft* magazine, a means of inspiring builder confidence.

Why not? The Doerle is a fun radio and can be built for little or nothing if you have a good junk box, or are a good scrounger at a flea market. Choose one of the many circuits shown in this article. I suggest you make it on a piece of plywood and use a grounded aluminum panel to reduce the effects of hand capacitance. Probably the ac circuit is best today, as dc tubes are microphonic, hard to find, and require a hum-free filament supply. The ac circuit can use any of the following tube types: 227, 56, 76, 6C5, 6J5, or 6C4. Surely you have two of these in your junk box!

The audio transformer can be a replacement “three-to-one” type, and the rf choke can be a 2.5 millihenry pi-wound affair. If you feel like a pioneer, you can wind the coils on 4-prong tube bases or other insulating material, about 32 mm (1-1/4 inches) in diameter. The lucky scrounger might come up with a set of commercially wound coils made for these little receivers! As for the rf choke, the original Doerle used a home made one. It consisted of 300 turns of 0.13-mm (no. 36) double silk covered wire, close wound on a 13-mm (1/2-inch) diameter wood dowel rod.

Operation of the choke can be checked by pressing the earphone cord in your hand when the set is operating. If no change occurs in the received signal, the choke is doing its duty.

Today's radio spectrum is far different from what it was in the early thirties. Hearing a signal was a significant feat then; today the powerful signals and heavy congestion of the short-wave channels make reception a problem of receiver overload. The little Doerle (in common with all regenerative receivers) is highly susceptible to signal

overload. The pigmy antenna-coupling capacitor helps, but you should use a short antenna with this set — 5-6 meters (15-20 feet) of wire is sufficient. A longer antenna will lead to severe receiver blocking and overload. To prevent instability, moreover, the antenna should be firmly supported so it won't swing about in the wind. A moving antenna will affect the tuning of the receiver. An indoor antenna is suggested.

SHORT WAVE SETS 

Sets Which Work At Your Command

And NOW The *Electrified* Official Doerle

 2 And 3 Tube Receivers

[illegible]

Improved Circuit and Design

Despite the remarkable performance of the Duoflex receivers, our technical staff felt that they could obtain better results by making slight modifications of the original type. In the first type, the Tule Signal Gripper, both the new A.C. and 2-volt models, in the second model, the first type 30 H. F. tube was replaced by a type 34, which is a special-purpose grid B. F. amplifier. In the A. C. model, a type 58 triode-triac, high gain H. F. tube is employed. Furthermore, in the latter model the antenna trimmer condenser has been eliminated through the use of inductive coupling. The detector plug-in coils are of the six-prong type, each having three separate windings. This means that the R. F. Stage is inductively coupled to the detector.

Yet, despite these various changes, we have not increased the price of these receivers,

By special arrangements with the publishers of Short Wave Craft, we have been given the *exclusive right to manufacture and sell the Official Doerle Receivers*, both the earlier 2-volt and the latest A. C. models—so that now, all short-wave enthusiasts who have ever wished to own any of these fine sets can buy them without the slightest doubt in their mind but what they will perform 100%. This means that all the usual "bugs" have been ironed out by us in such a way that in practically every location anywhere, they will "do their best."

Only First-Class Parts Are Used

It may be possible to buy the parts or completed sets at a lower price—we admit this at once—but without concern. For we have used only the best parts available in the construction of our sets. We have done away with all usual "boom" parts which are incident to the use of old-fashioned, only because they are old-fashioned, tuning condensers, and that means they are used! These sets could be produced for a considerably less amount if we used cheaper condensers. We refrained from doing so, however, because they COULD NOT GUARANTEE.

If you are skeptical of the results obtainable with these receivers, read the letters from our many short-wave fans and friends printed on the opposite page.

Our Own Tests

Every one of these Duane receivers, without exception, is tested in our laboratory under actual operating conditions. We refrain from giving you the acoustical list of stations which we ourselves have logged during the course of our tests; for we do not wish to let our enthusiasm run away with us. We would much rather have you and our many other able friends take advantage of the results. Incidentally, we have yet to receive a single complaint on any of these sets although we have sold many hundreds of them. Each receiver is accompanied by schematic diagram and wiring blueprint, as well as a pamphlet

[illegible]

No. 2149 Special Short-Wave Hum-Free A. C. Power Pack, including 280 tube. **\$6.27**

building a Doerle receiver? I can't think of any circuit that will provide more simple pleasure in construction and use than the Doerle circuit. You'll be surprised at how the signals pour in on the little set. The signals will not be loud, as the circuit lacks audio power. But the signals will be there, and the sensitivity of a regenerative set is equal to that of the more expensive receivers of 1978! With patience and experience, the Doerle receiver will



NO. 2174.	Electrified 2 Tube 13,000 Miles Doorle Receiver, completely wired and tested, one tube. Measures 9" long x 2 1/2" high x 5 1/2" deep. Ship w. 5 lbs.	\$9.47
YOUR PRICE		
NO. 2175.	Electrified 3 Tube 12,000 Miles Doorle Receiver in kit form, two tubes, but including blueprints and instructions.	\$8.27
YOUR PRICE		
NO. 2176.	Complete set of tubes for above—5A, operation—57 and one—56 for A. C. operation, one—77 for B. C. operation—37 for factory operation.	\$1.82
NO. 2177.	Electrified 3 Tube Doorle Signal Gripper, completely wired and tested, one tube. Measures 10 1/2" long x 7" high x 8 1/2" wide. Ship w. 5 lbs.	\$14.22
YOUR PRICE		
NO. 2178.	Electrified 3 Tube Doorle Signal Gripper in kit form, including blueprints and one tube. Ship w. 7 lbs.	\$12.77
YOUR PRICE		
NO. 2179.	Complete set of tubes, either one—5A, one—56 and one—56 for A. C. operation, one—77, one—77—none—37 for factory operation.	\$2.72
YOUR PRICE		

NO. 2140.	TWO TUBE 12,500 MIC. 2-VOLT DOORIE SHORT WAVE RECEIVER KIT, w/40 loudspeaker and tested. Ship. w/ 5 lbs.	\$8.92
NO. 2141.	TWO TUBE 12,500 MIC. 2-VOLT DOORIE SHORT WAVE RECEIVER KIT, w/40 loudspeaker and tested. Ship. w/ 5 lbs.	\$7.72
NO. 2142.	COMPLETE ACCESSORIES, including 2 N. 6 tubes; one set of Brander Headphones; 2 N. 6 dry cells; 2 magnatic Loudspeakers; 1 set of instructions. Ship. w/ 22 lbs.	\$5.42
NO. 2143.	THREE TUBE 2-VOLT DOORIE SET, com- plete w/ everything you need to operate. Ship. w/ 11 lbs.	\$11.00
NO. 2144.	THREE TUBE 2-VOLT DOORIE SET IN KIT FORM, with blueprint instructions. Ship. w/ 7 lbs.	\$10.52
NO. 2145.	COMPLETE ACCESSORIES, including 2 N. 6 tubes; one set of Brander Headphones; 2 N. 6 dry cells; 2 standard 45-volt B. batteries; 1 set of Magnatic Loudspeakers; 22 lbs.	\$11.00

of either one of books illustrated
herewith—**FREE OF CHARGE**
—with the purchase of any of
the short-wave receivers listed
in this advertisement.

Book No. 886 explains in a
most thorough-going manner the
ways and means of obtaining an
amateur transmitting license.
Furthermore, all government
rules regulating amateur transmissions are
reviewed. Book 880 is
comprehensive and thorough
compilation of the most
prominent short-wave receiv-
er circuits published during
period of two years. Build
up your radio library with
one of these books.

OPRAC
HOW TO
MAKE
SHORT-
WAVE
RECEIVERS

Book No. 831

THE AMATEUR
RADIO OPERATOR

Book No. 880

Book No. 886

FREE 116 page Radio and Short Wave Treatise. 100 hook-ups, 1,000 illustrations. Enclose 4c for postage. Treatise sent by return mail.

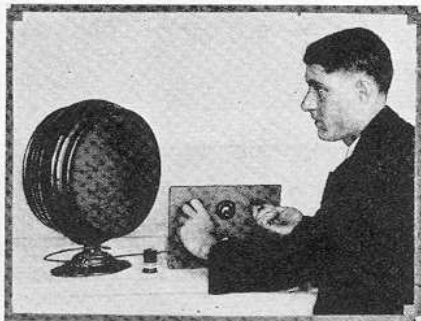


Fig. 4. The only published photograph of Mr. Doerle was in *Short Wave Craft* magazine for November, 1932. He is shown demonstrating his new DX receiver which was capable of driving a loud-speaker. Doerle's article describing the receiver was entitled "A 3-Tube Signal Gripper."

perform wonders for you and you'll gain appreciation of some of the heritage that's behind today's hobby of amateur radio.

Further reading


The formative years of radio (or electronics as we know it today) make interesting reading for newcomers and old timers alike. The bibliography that follows lists some articles published by *ham radio* and *Ham Radio Horizons* that describe how it used to be. Your local library probably has copies of some of the early radio magazines. During those years you could find these radio magazines on the news stands sandwiched between *Collier's*, *Liberty*, and *The Women's Home Companion*.

Bibliography

Nagle, John J. K4KJ, "Those Good Ol' Radio Magazines," *Ham Radio Horizons*, December 31, 1977, pages 38-47.
 Orr, William I., W6SAI, "1929 — 1941, The Golden Years of Amateur Radio," *ham radio*, April, 1976, pages 34-38.
 Orr, William I., W6SAI, "The Golden Years of Radio," *Ham Radio Horizons*, May, 1978, pages 40-43.
 Orr, William I., W6SAI, "The Golden Years of Radio — The Way it Was — 40 Years Ago," *Ham Radio Horizons*, March, 1977, pages 32-36.

HRH

Touch-Tone Decoders

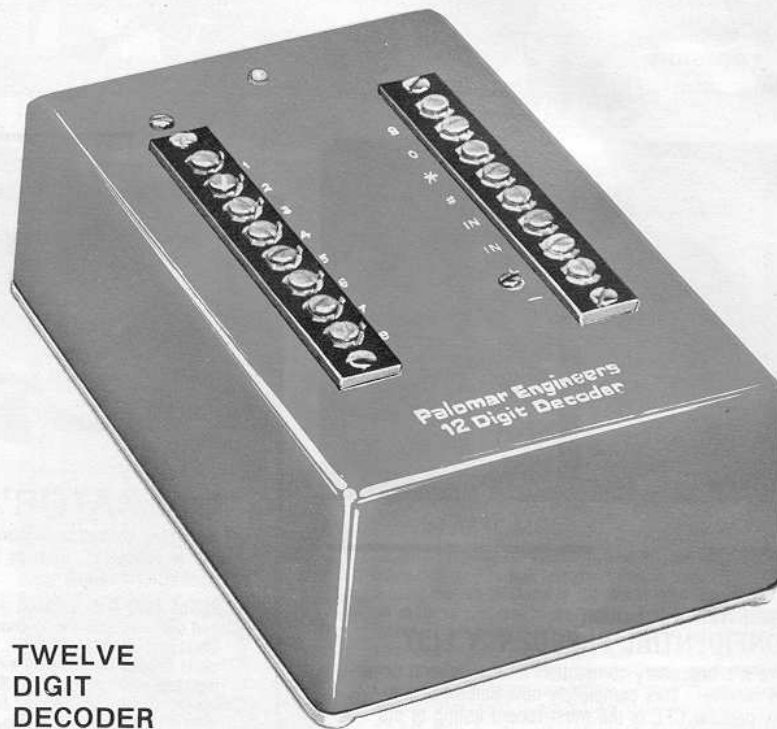


**TWELVE
DIGIT
DECODER**
\$145.00

- Decodes digits 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, * and #.
- Twelve 5-volt output lines.
- Isolated 5000 ohm input.
- Operates from any DC voltage + 12 to + 30 volts.
- Output drives TTL logic or relays.



MODEL T2 \$49.95

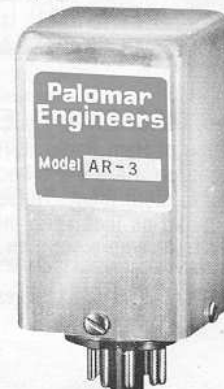- Decodes one Touch-Tone digit.
- Available for digits 1, 2, 3, 4, 5, 6, 7, 8, 9, 0, *, and #. Also for digits A, B, C, D.
- Relay output SPST ½ amp.
- Operates on any DC voltage + 12 to + 30 volts.



MODEL AR-3 \$49.95

- Sequence decoder.
- Connects to 12-digit decoder.
- Three digits must appear in correct order and timing to close output relay.
- For foolproof secure signalling.

Send for free brochure. ORDER TODAY. Add \$2 shipping/handling. Add sales tax in Calif.

Palomar Engineers

Box 455, Escondido, CA. 92025 • Phone: [714] 747-3343